

Pseudo-Random Waveforms and Comb Calibration Signals

Evans Paschal

9/12/05

This note describes a technique for generating a signal which has a comb spectrum. It contains many harmonics of a given base frequency, and the amplitudes of all the harmonics are equal. A signal like this is a useful calibration signal when applied to the input of an amplifier under test. As long as the amplifier passes the signal without distortion, we can measure the gain and frequency response of the amplifier in one step. That is, since the amplitude and frequency of each component of the input comb signal is known, by measuring the amplitudes of these components in the output we can find the gain of the amplifier as a function of frequency, as shown in Figure 1.

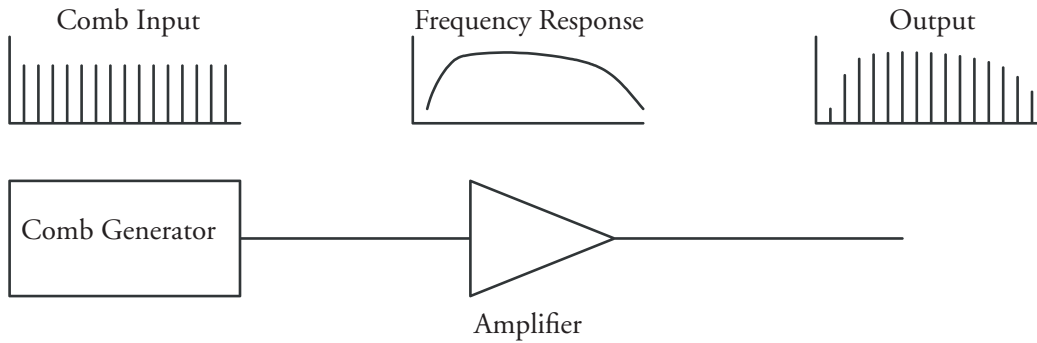


Figure 1. Using comb signal to measure amplifier frequency response.

Perhaps the simplest way to generate a comb signal is to use a short repetitive pulse. The pulse repetition frequency f_0 is the base frequency of the comb. As long as the width of the pulse is sufficiently narrow, the amplitudes of the harmonic components in the waveform at multiples of f_0 can be made as uniform as desired; that is, the envelope of the comb spectrum can be as flat as needed. This approach has a major limitation, however: all the power of the signal is contained in the short pulse; the rest of the time the waveform is zero. To obtain useful power in each of the comb components a very large pulse must be used, and such a pulse will be clipped in the amplifier. Once it's clipped, it can't be used to measure amplifier frequency response.

The approach we'll follow here is to generate a pseudo-random waveform. This is a signal whose waveform appears to be random over short intervals, but which is actually deterministic and repeats over a cycle time t_0 . It has frequency components at multiples of $f_0 = 1/t_0$. And the peak to rms ratio of the waveform is low, meaning it is much less likely to be clipped in the amplifier.

A pseudo-random waveform, also known as pseudo-random noise, is the output of a pseudo-random binary sequence generator. This is often implemented as a shift register with feedback as shown in Figure 2.

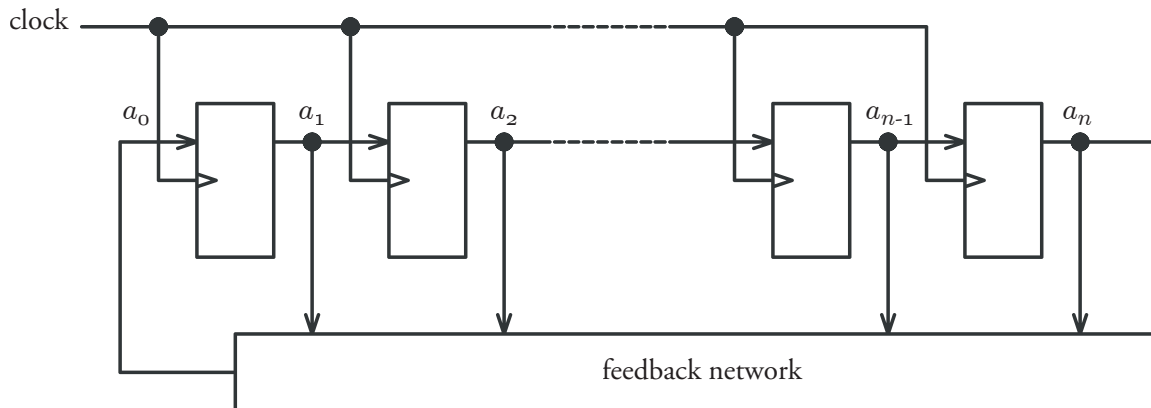


Figure 2. Shift register with feedback

The shift registers are clocked such that, at time p , $a_i(p) = a_{i-1}(p-1)$. That is, the previous state at a_{i-1} appears as state a_i after the clock pulse. State a_0 at the input to the shift register is some function of states a_1, \dots, a_n , or, equivalently, of previous a_0 's, as

$$a_0(k) = f(a_1(k), a_2(k), \dots, a_n(k)) = f(a_0(k-1), a_0(k-2), \dots, a_0(k-n)). \tag{1}$$

The usual feedback is “linear” feedback of the form

$$a_0(k) = c_1 a_1(k) \oplus c_2 a_2(k) \oplus \dots \oplus c_n a_n(k), \tag{2}$$

where each c_i is 0 or 1, depending if state a_i is fed back or not, and \oplus indicates modulo-2 summation (that is, the XOR function).

With the proper choice of c_i 's we can generate a maximal length sequence, whose sequence length is $m = 2^n - 1$, as shown in Figure 3. Note that an n -stage shift register has a total of 2^n different states, but that the all-zero state makes $a_0 = 0$, which gives the all-zero state again. Only at most $2^n - 1$ other states can be in a sequence. Our design must prevent the shift register from starting in the all-zero state.

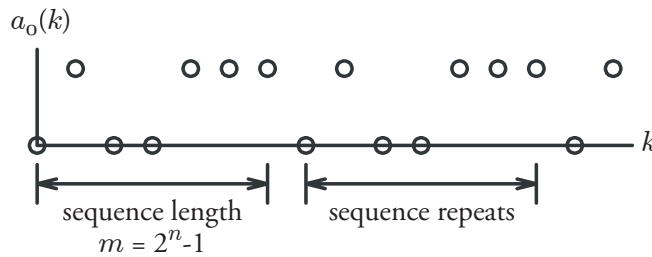


Figure 3. Maximal length shift register sequence

A maximal length shift register sequence has several interesting statistical properties.* For instance, the number of zeros and ones is nearly equal (in fact, there is always exactly 1 more ones than zeros). There are two runs (of constant value) of length p for every run of length $p+1$. And, most important for our use, the autocorrelation function

$$R(i) \equiv \frac{1}{m} \sum_{k=0}^{m-1} a_0(k) * a_0(i-k) \tag{3}$$

is two-valued, with a peak at 0 phase (and multiples of the sequence length m) and a very small value elsewhere, as shown in Figure 4. (Note that we have considered the sequence to take on the values -1 and 1 here, rather than 0 and 1.)

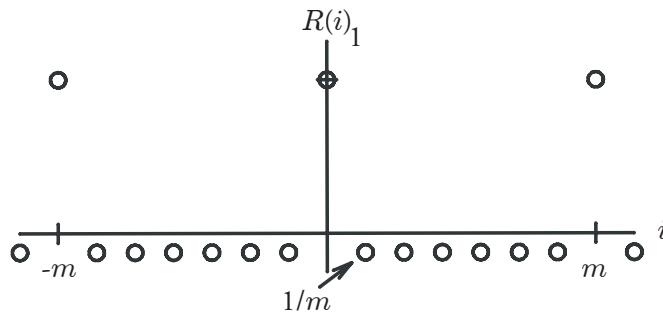


Figure 4. Autocorrelation of maximal length sequence

*For further details, the reader is referred to the definitive work: *Shift Register Sequences*, Solomon W. Golomb, Holden-Day, 1967.

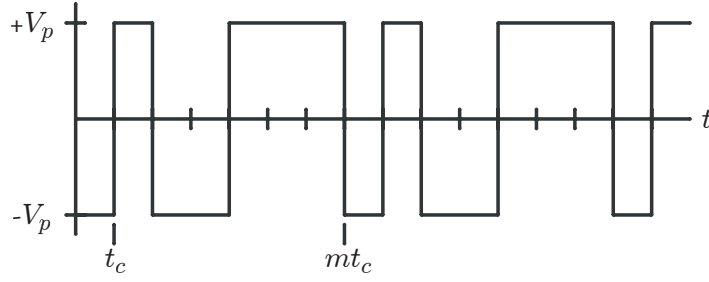


Figure 5. Shift register output viewed as a voltage waveform

Now consider the output of the shift register as a voltage waveform $v(t)$ as a function of time, as shown in Figure 5. The shift register is clocked every t_c seconds. The waveform $v(t)$ can have two values, either $+V_p$ or $-V_p$, and can change only at clock transitions. The waveform repeats every mt_c seconds. The autocorrelation $R(\tau)$ of this waveform is given by Equation 4, where

$$\begin{aligned}
 R(\tau) &= \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} v(t)v(\tau - t)dt \\
 &= V_p^2 \left[\left(1 + \frac{1}{m}\right) \Lambda\left(\frac{\tau}{t_c}\right) - \frac{1}{m} \Pi\left(\frac{\tau}{mt_c}\right) \right] * \sum_{k=-\infty}^{\infty} \delta(\tau - kmt_c)
 \end{aligned} \quad (4)$$

the $*$ operator indicates convolution. $R(\tau)$ is shown in Figure 6.

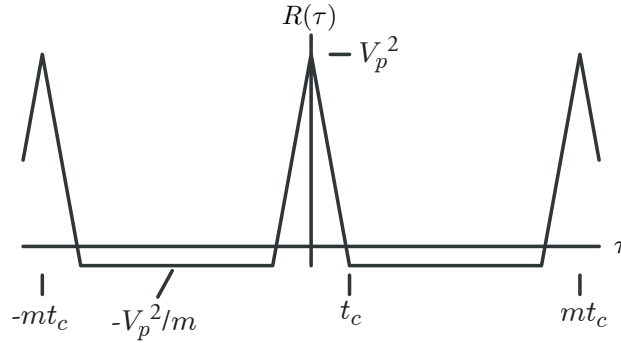


Figure 6. Autocorrelation of shift register output

Note that this is the same as the autocorrelation of a short repetitive pulse, except for the small negative value $-V_p^2/m$. The power spectrum of the shift register output $G(f)$ is the Fourier transform of the autocorrelation function, as

$$\begin{aligned}
 G(f) &= F\{R(\tau)\} \\
 &= V_p^2 \left[\left(\frac{m+1}{m^2}\right) \text{sinc}^2(ft_c) - \frac{1}{m} \text{sinc}(f mt_c) \right] \cdot \sum_{k=-\infty}^{\infty} \delta\left(f - \frac{k}{mt_c}\right),
 \end{aligned} \quad (5)$$

where the sinc function is defined by $\text{sinc}(x) \equiv \sin(\pi x)/\pi x$. The power spectrum $G(f)$ is zero everywhere except at multiples of $1/mt_c$, that is, at harmonics of the sequence repetition rate. If we filter the signal around one of these harmonics (including power at negative as well as positive frequency), we find the rms voltage of the spectral component at a given harmonic frequency is

$$V(0) = V_p/m, \quad (6)$$

$$\text{and } V(kf_0) = V_p \frac{\sqrt{2}(m+1)^{1/2}}{m} \text{sinc}(k/m), \quad k = 1, 2, \dots, \quad (7)$$

where $f_0 = 1/mt_c$ is the sequence repetition rate. The term $V(0)$ is a small dc voltage, which we can ignore (use capacitive coupling to the rest of the circuit). The other components are all multiples of the comb frequency f_0 . (Note: while we know the rms amplitudes of the comb components, we don't know their relative phases, which have no simple relationship.)

Design Procedure

1. The bandwidth of the amplifier to calibrate is known. Choose the frequency f_o and factor k such that the frequency comb from f_o to kf_o spans the frequency interval of interest. (If a finer comb spacing is desired, choose the comb spacing f_o and find integers j and k such that jf_o to kf_o spans the interval of interest.) For example, assume we want to measure our amplifier response from 100 Hz to 30 kHz. If we chose $f_o = 100$ Hz, then the comb component at 30 kHz will be the 300th component, or $k = 300$.

2. Decide how flat the comb needs to be. The rms voltage of higher-frequency components is proportional to $\text{sinc}(k/m)$. For example, assume we want the 300th component to be down no more than 0.5 dB (0.944) from the first component. We need $\text{sinc}(k/m) > 0.944$. For $k = 300$ we find $m \geq 1613$.

3. The sequence length m must be of the form $2^n - 1$. Find the integer n that gives an m greater than the minimum found in the previous step. (Making n even bigger will, of course, make the comb even flatter, but at the expense of a greater peak voltage for a given component rms voltage.) For example, for $m \geq 1613$ we find $n = 11$, giving $m = 2047$, and $\text{sinc}(300/m) = 0.965 = -0.31$ dB.

4. Calculate the shift register clock frequency $f_c = mf_o$. For example, $2047 \times 100 \text{ Hz} = 204.700$ kHz. This may not be a convenient frequency. Depending on how much effort we want to go to, we may need to compromise our original specifications and adjust f_o to give a better clock frequency.


5. Finally, calculate the rms voltage of each comb component using Equation 7. For example, assume we use the capacitive-coupled output of a shift register built with 5-volt logic. The output swings from 0 to +5 V, so the ac signal after the capacitor will swing from -2.5 V to +2.5 V, or $V_p = 2.5$ V. For $m = 2047$, we find $V(100 \text{ Hz}) = 78.1$ mV (and $V(30 \text{ kHz}) = 75.4$ mV). We may need to amplify or attenuate the 2.5 V “square-wave” output of the shift register to get the amplitude we need.

Note the advantage of the pseudo-random comb generator in the example above. If we had generated the comb signal using a short rectangular pulse, we would have used a pulse 4.89 μs wide ($1/mf_o$), repeated every 10 ms. To get the same 78 mV component amplitude, however, the short pulse would need an amplitude of $m^{1/2}V_p$ or 113 V! Our amplifier would need an additional 33 dB of headroom to pass this pulse without distortion. The problem with a short pulse, of course, is that all the energy of the signal is contained in the pulse, whereas the pseudo-random waveform spreads the energy out and is always running at constant power. In terms of the peak voltage required for a given component amplitude, the pseudo-random waveform is the optimum solution.

Sample Designs


Figures 7 and 8 show two comb filter designs that are currently used at field stations for calibrating ELF and VLF receivers. The circuit in Figure 7 is used in the Noise Survey project receivers (Tony Fraser-Smith's experiment). The comb generator is implemented in 4000-series CMOS logic running from a 15-volt supply. Three 4015 4-stage shift registers are wired in series to give a 12-bit shift register; only the first 11 bits are used ($m = 2047$). Note that the feedback logic here uses XNOR (inverting XOR) logic. This works because, while we're loading the inverse feedback into the shift register, and thus looking at the Q-bar outputs instead of the Q outputs, the XOR of two Q-bar outputs gives the same result as the XOR of two Q outputs. We're really generating the inverse of the sequence. In this design, the all-ones state is the state to be avoided. This is accomplished by using the 4015 reset inputs to be sure the shift register starts off in the all-zeros state. The clock frequency required is synthesized using a divide-by- m counter and a phase-locked-loop referenced to an external standard. Since this circuit is designed to calibrate ELF as well as VLF receivers, with the ELF comb going as low as 10 Hz, dc coupling is used for the comb signal. The Disable Offset input to the low-pass filter compensates for the dc offset while the shift register is held off in its all-zeros state.

Figure 8 shows the comb calibrator in the new HAIL2 preamps currently being deployed by Stanford. In this circuit the pseudo-random sequence is generated by a PIC12F629 microprocessor. The microprocessor generates the maximum length sequence of a 10-stage shift register ($m = 1023$). With a crystal oscillator input of $f_x = 8.192$ MHz, the internal microprocessor clock runs at $f_x/4 = 2.048$ MHz. The cycle time for the shift register is 8 microprocessor instructions, so the virtual shift register clock is $f_c = f_x/32 = 256$ kHz. With a sequence length of $m = 1023$, the comb components are spaced every 250.244 Hz, and the spectral envelope is down by 0.22 dB at 32 kHz. The desired comb spacing was $f_o = 250.000$ Hz. This would have required a crystal oscillator frequency of 8.184 MHz. This is not available in an off-the-shelf oscillator, so the closest available frequency was used. Rather than using XOR (or XNOR) feedback of the register contents to determine the next input bit to the shift register, the program in the microprocessor tests the shift register output and, if zero, XORs the feedback value into the register (broadside, as it were). We can think of this as running the circuit in Figure 2 in time-reversed order.

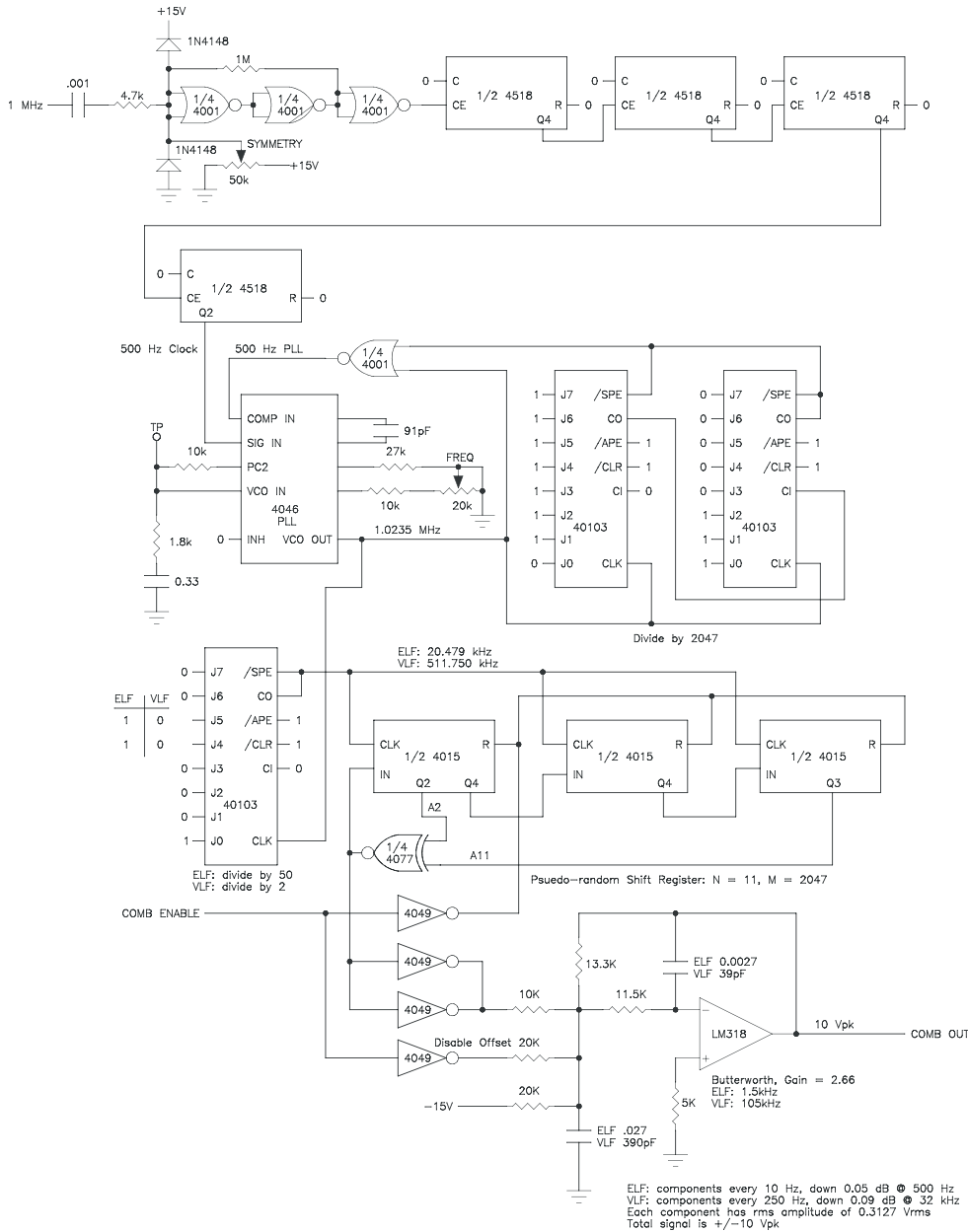

Noise Survey ELF/VLF Comb Generator
E. Paschal 03/09/81 Stanford University

Figure 7. Comb generator using 15-volt 4000-series CMOS logic.

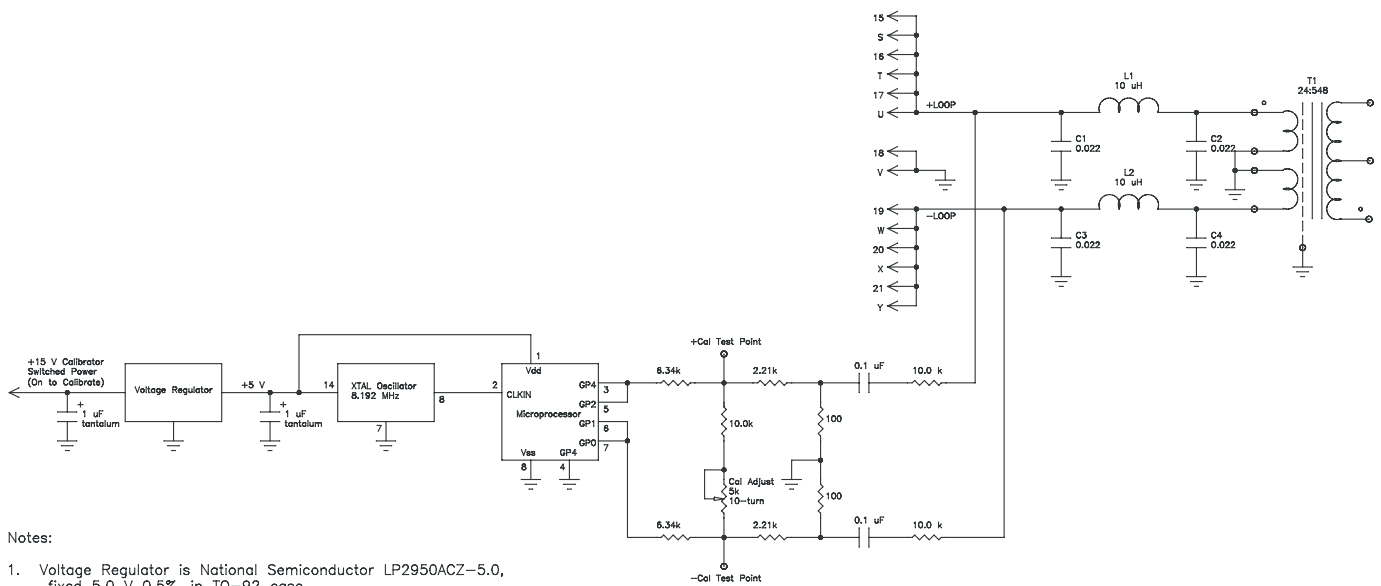

Notes:

1. Voltage Regulator is National Semiconductor LP2950ACZ-5.0, fixed 5.0 V 0.5%, in TO-92 case.
2. Crystal Oscillator is 8.192 MHz 100ppm in 14-pin DIP package, EPSON SG-51 8.1920MC or similar.
3. Microprocessor is Microchip PIC12F629 in 8-pin DIP.
4. 1 uF tantalum capacitors at voltage regulator can be 20 or 35 V units, Kemet T350A105M035AS, for instance.
5. All resistors RN55D 1% metal film.
6. 0.1 uF capacitors X7R (not Z5U) ceramic 5%, any voltage.

Comb Calibrator generates calibration components of equal amplitude every 250 Hz throughout VLF spectrum. Adjust "Cal Adjust" pot for 1 V peak-to-peak at +Cal and -Cal testpoints (or 2 V p-p between them). This will give each component an amplitude of 1.00 mV rms at the 10 k cal resistors (equivalent to 0.69 pT or 208 uV/m when using 4.9m square 1-ohm 1-mH loop).

HAIL2 VLF Line Receiver Comb Calibration Generator Rev 1
E. Paschal 2/28/04 WHISTLER RADIO SERVICES

Figure 8. Comb generator implemented with a microprocessor.

Appendix 1: Program to List Maximal-Length Sequence Feedback Taps

The following C language program lists all XOR feedback taps that give maximal-length shift register sequences for $n = 3$ to n_{max} (nominally 16). The (edited) output of this program is listed in Appendix 2.

```
/*PRSeqList.cpp
*
* Pseudo-random shift-register sequence feedback list program
* E. Paschal
* 2/19/04
*
* This program is used to list feedback taps for shift registers which
* give maximal-length sequences using XOR feedback. The program lists
* all feedback taps for shift register lengths from 3 to nmax.
*/

#include <stdio.h>

/* Global variables */
int nmax; /* maximum shift-register length, 3 to 31 */
int n; /* current shift-register length */
unsigned long regist; /* shift register, up to 31 bits */
unsigned long feedbk; /* feedback taps */
unsigned long rmask; /* register mask, 0s except n 1s on right end */
unsigned long m; /* (2**n)-1 = maximal length (= rmask) */
unsigned long mp1; /* 2**n */
unsigned long count; /* shift counter */
unsigned long soluts; /* number of maximal-length solutions */
FILE *listfile;

int main()
{
    listfile = fopen("Seqlist.txt","a");
    nmax = 16; /* don't make it too big unless you have
                a fast machine. must be 31 or less */
    for (n = 3; n <= nmax; n++) { /* do next sequence length */
        int i; /* loop counters */
        rmask = 0;
        for (i = 0; i < n; i++) {
            rmask = (rmask << 1) + 1; /* shift in n 1s to mask */
        }
        m = rmask; /* 2**n -1 */
        mp1 = m + 1; /* 2**n */
        soluts = 0; /* reset solution count for this n */
        printf("Registers n = %d, Sequence length m = %d\n",n,m);
        fprintf(listfile,"Registers n = %d, Sequence length m = %d\n",n,m);
        /* test all possible feedbk's */
        /* first feedback mask is '1000..000' */
        for (feedbk = m/2; feedbk < mp1-1; feedbk++) {
            regist = 0; /* start with register clear */
            for (count = 1; count <= mp1; count++) { /* shift till back to 0 */
                unsigned long regtemp;
                int bitct;
                int j;
                regtemp = regist & feedbk; /* mask feedback bits */
                bitct = 0;
                for (j = 0; j < n; j++) { /* count masked bits set */
                    if (regtemp & 1) bitct++;
                    regtemp = regtemp >> 1;
                }
                regist = regist << 1; /* shift register left */
                /* shift in a 1 if even feedback bits */
                if ((bitct & 1) == 0) regist++;
                regist = regist & rmask; /* mask to n bits */
                if (regist == 0) break; /* done when we're back to 0 */
            }
            if (count == m) {
                soluts++;
                printf ("Feedback %6x = ",feedbk);
                fprintf (listfile,"Feedback %6x = ",feedbk);
                regist = feedbk;
                for (i = 0; i < n; i++) {
                    regist = regist << 1;
                    printf ("%1x", (mp1 & regist) >> n);
                    fprintf (listfile,"%1x", (mp1 & regist) >> n);
                }
                printf ("\n");
                fprintf (listfile,"\n");
            }
        }
        printf("Number of maximal-length solutions = %d\n\n",soluts);
        fprintf(listfile,"Number of maximal-length solutions = %d\n\n",soluts);
    }
    return(0);
}
```

Appendix 2: Partial Listing of Maximal-Length Sequence Feedback Taps

This listing shows feedback taps that will give maximal-length pseudo-random sequences for shift registers from 3 to 16 bits long. For instance, the feedback used in the comb generator in Figure 7 (bits a_2 and a_{11}) is shown below in bold as the first entry in the table for $n = 11$. Note that for many shift register lengths it is possible to generate a maximal-length sequence using only two feedback taps. However, for lengths $n = 8, 12, 13, 14,$ and 16 , four taps must be used.

Registers $n = 3$, Length $m = 7$	Feedback 10d = 100001101
Feedback 5 = 101	Feedback 110 = 100010000
Feedback 6 = 110	Feedback 116 = 100010110
Number of solutions = 2	Feedback 119 = 100011001
	Feedback 12c = 100101100
Registers $n = 4$, Length $m = 15$	Feedback 12f = 100101111
Feedback 9 = 1001	Feedback 134 = 100110100
Feedback c = 1100	Feedback 137 = 100110111
Number of solutions = 2	Feedback 13b = 100111011
	...
Registers $n = 5$, Length $m = 31$	Feedback 1da = 111011010
Feedback 12 = 10010	Feedback 1dc = 111011100
Feedback 14 = 10100	Feedback 1e3 = 111100011
Feedback 17 = 10111	Feedback 1e5 = 111100101
Feedback 1b = 11011	Feedback 1e6 = 111100110
Feedback 1d = 11101	Feedback 1ea = 111101010
Feedback 1e = 11110	Feedback 1ec = 111101100
Number of solutions = 6	Feedback 1f1 = 111110001
	Feedback 1f4 = 111110100
Registers $n = 6$, Length $m = 63$	Feedback 1fd = 111111101
Feedback 21 = 100001	Number of solutions = 48
Feedback 2d = 101101	
Feedback 30 = 110000	Registers $n = 10$, Length $m = 1023$
Feedback 33 = 110011	Feedback 204 = 1000000100
Feedback 36 = 110110	Feedback 20d = 1000001101
Feedback 39 = 111001	Feedback 213 = 1000010011
Number of solutions = 6	Feedback 216 = 1000010110
	Feedback 232 = 1000110010
Registers $n = 7$, Length $m = 127$	Feedback 237 = 1000110111
Feedback 41 = 1000001	Feedback 240 = 1001000000
Feedback 44 = 1000100	Feedback 245 = 1001000101
Feedback 47 = 1000111	Feedback 262 = 1001100010
Feedback 48 = 1001000	Feedback 26b = 1001101011
Feedback 4e = 1001110	
Feedback 53 = 1010011	...
Feedback 55 = 1010101	Feedback 3aa = 1110101010
Feedback 5c = 1011100	Feedback 3ac = 1110101100
Feedback 5f = 1011111	Feedback 3b1 = 1110110001
Feedback 60 = 1100000	Feedback 3be = 1110111110
Feedback 65 = 1100101	Feedback 3c6 = 1111000110
Feedback 69 = 1101001	Feedback 3c9 = 1111001001
Feedback 6a = 1101010	Feedback 3d8 = 1111011000
Feedback 72 = 1110010	Feedback 3ed = 1111101101
Feedback 77 = 1110111	Feedback 3f9 = 1111111001
Feedback 78 = 1111000	Feedback 3fc = 1111111100
Feedback 7b = 1111011	Number of solutions = 60
Feedback 7e = 1111110	
Number of solutions = 18	Registers $n = 11$, Length $m = 2047$
	Feedback 402 = 1000000010
Registers $n = 8$, Length $m = 255$	Feedback 40b = 10000001011
Feedback 8e = 10001110	Feedback 415 = 10000010101
Feedback 95 = 10010101	Feedback 416 = 10000010110
Feedback 96 = 10010110	Feedback 423 = 10000100011
Feedback a6 = 10100110	Feedback 431 = 10000110001
Feedback af = 10101111	Feedback 432 = 10000110010
Feedback b1 = 10110001	Feedback 438 = 10000111000
Feedback b2 = 10110010	Feedback 43d = 10000111101
Feedback b4 = 10110100	Feedback 446 = 10001000110
Feedback b8 = 10111000	
Feedback c3 = 11000011	...
Feedback c6 = 11000110	Feedback 7c8 = 11111001000
Feedback d4 = 11010100	Feedback 7cb = 11111001011
Feedback e1 = 11100001	Feedback 7cd = 11111001101
Feedback e7 = 11100111	Feedback 7d3 = 11111010011
Feedback f3 = 11110011	Feedback 7d6 = 11111010110
Feedback fa = 11111010	Feedback 7da = 11111011010
Number of solutions = 16	Feedback 7e6 = 11111100110
	Feedback 7e9 = 11111101001
Registers $n = 9$, Length $m = 511$	Feedback 7f2 = 11111110010
Feedback 108 = 100001000	Feedback 7f4 = 11111110100
	Number of solutions = 176

Registers n = 12, Length m = 4095

Feedback 829 = 100000101001
Feedback 834 = 100000110100
Feedback 83d = 100000111101
Feedback 83e = 100000111110
Feedback 84c = 100001001100
Feedback 868 = 100001101000
Feedback 875 = 100001110101
Feedback 883 = 100010000011
Feedback 88f = 100010001111
Feedback 891 = 100010010001

...

Feedback f47 = 1111101000111
Feedback f71 = 111101110001
Feedback f88 = 111110001000
Feedback f8d = 111110001101
Feedback f93 = 111110010011
Feedback fb8 = 111110111000
Feedback fcc = 111111001100
Feedback fdd = 111111011101
Feedback fde = 111111011110
Feedback fe4 = 111111100100

Number of solutions = 144

Registers n = 13, Length m = 8191

Feedback 100d = 1000000001101
Feedback 1013 = 1000000010011
Feedback 101a = 1000000011010
Feedback 1029 = 1000000101001
Feedback 1032 = 1000000110010
Feedback 1037 = 1000000110111
Feedback 1045 = 1000001000101
Feedback 1046 = 1000001000110
Feedback 104f = 1000001001111
Feedback 1052 = 1000001010010

...

Feedback 1fab = 1111110101011
Feedback 1fb0 = 111110110000
Feedback 1fc1 = 111111000001
Feedback 1fc4 = 1111111000100
Feedback 1fc8 = 111111001000
Feedback 1fd5 = 111111010101
Feedback 1fda = 1111111011010
Feedback 1ff1 = 111111110001
Feedback 1ffb = 111111111011
Feedback 1ffe = 1111111111110

Number of solutions = 630

Registers n = 14, Length m = 16383

Feedback 2015 = 10000000010101
Feedback 201c = 10000000011100
Feedback 2029 = 10000000101001
Feedback 202f = 10000000101111
Feedback 203d = 10000000111101
Feedback 2054 = 10000001010100
Feedback 2057 = 10000001010111
Feedback 205d = 10000001011101
Feedback 205e = 10000001011110
Feedback 2067 = 10000001100111

...

Feedback 3f9f = 11111110011111
Feedback 3fa6 = 11111110100110
Feedback 3faa = 11111110101010
Feedback 3fb8 = 11111110111000
Feedback 3fc5 = 1111111000101
Feedback 3fc6 = 1111111000110
Feedback 3fcf = 1111111001111
Feedback 3fe2 = 1111111100010
Feedback 3fe8 = 1111111101000
Feedback 3ff3 = 11111111110011

Number of solutions = 756

Registers n = 15, Length m = 32767

Feedback 4001 = 100000000000001
Feedback 4008 = 100000000001000
Feedback 400b = 100000000001011
Feedback 4016 = 100000000010110
Feedback 401a = 100000000011010
Feedback 402f = 100000000101111
Feedback 403b = 10000000011011
Feedback 4040 = 100000001000000
Feedback 4043 = 100000001000011
Feedback 4049 = 100000001001001

...

Feedback 7fb0 = 111111110110000
Feedback 7fb9 = 11111110111001
Feedback 7fbf = 111111110111111
Feedback 7fc8 = 111111111001000
Feedback 7fd9 = 11111111011001
Feedback 7fe3 = 111111111100011
Feedback 7fec = 111111111101100
Feedback 7ff4 = 11111111110100
Feedback 7ff7 = 111111111110111
Feedback 7ffe = 111111111111110

Number of solutions = 1800

Registers n = 16, Length m = 65535

Feedback 8016 = 1000000000010110
Feedback 801c = 1000000000011100
Feedback 801f = 1000000000011111
Feedback 8029 = 1000000000101001
Feedback 805e = 1000000001011110
Feedback 806b = 1000000001101011
Feedback 8097 = 1000000010010111
Feedback 809e = 1000000010011110
Feedback 80a7 = 1000000010100111
Feedback 80ae = 1000000010101110

...

Feedback ff41 = 1111111101000001
Feedback ff74 = 111111101110100
Feedback ff82 = 111111110000010
Feedback ff99 = 111111110011001
Feedback ff9a = 111111110011010
Feedback ff9c = 111111110011100
Feedbackffb8 = 111111110111000
Feedbackffd2 = 111111111010010
Feedbackfff5 = 111111111110101
Feedbackfff6 = 111111111110110

Number of solutions = 2048